

EE 316

Section 3

Pre Lab 06

By: Hannah Kelley

AC Signals, Transformers, and Bridge
Rectifiers

Introduction:

The goal of this laboratory is to explore AC signals, transformers, and diodes through theoretical calculations and circuit simulations. Different methods of representing and reporting AC voltages will be examined, including peak, peak-to-peak, and RMS values. The operation of transformers will also be analyzed using their turns ratios and voltage relationships. Finally, diode circuits will be simulated to investigate how sinusoidal AC signals can be rectified into DC signals.

Theoretical Analysis:

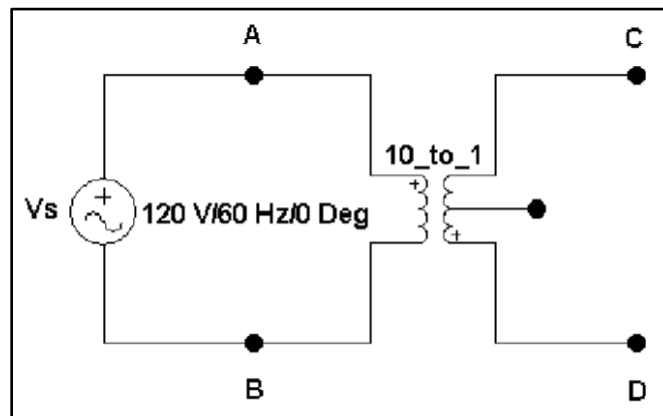


Figure #1: Basic Transformer Circuit (Lab Manual)

The basic transformer in Figure 1 has a peak voltage is approximately $120V * \sqrt{2} = 169.71V$.

This results in a peak-to-peak voltage of approximately $2 * V_{peak} = 339.41$. Using these voltages and a frequency of 60 Hz, the sinusoidal equation representing the input voltage at node A is:

$$V_A(t) = 169.71 \sin(2\pi 60t) V \quad (1)$$

Since the primary and secondary coils have a ratio of 10 to 1, the secondary voltage will have a peak value of $\frac{120}{10} = 12V_{rms}$ or $V_{peak} = 12 * \sqrt{2} = 16.97V$. Since the coils are perfectly coupled, node C will be in phase with node A while node D will be 180° out of phase with nodes A and C. This results in the following equations for nodes C and D.

$$V_C(t) = 16.97 \sin(2\pi 60t) V \quad (2)$$

$$V_D(t) = -16.97 \sin(2\pi 60t) = 16.97 \sin(2\pi 60t + 180^\circ) V \quad (3)$$

Figure 2 shows Equations 1, 2, and 3 each graphed over two cycles.

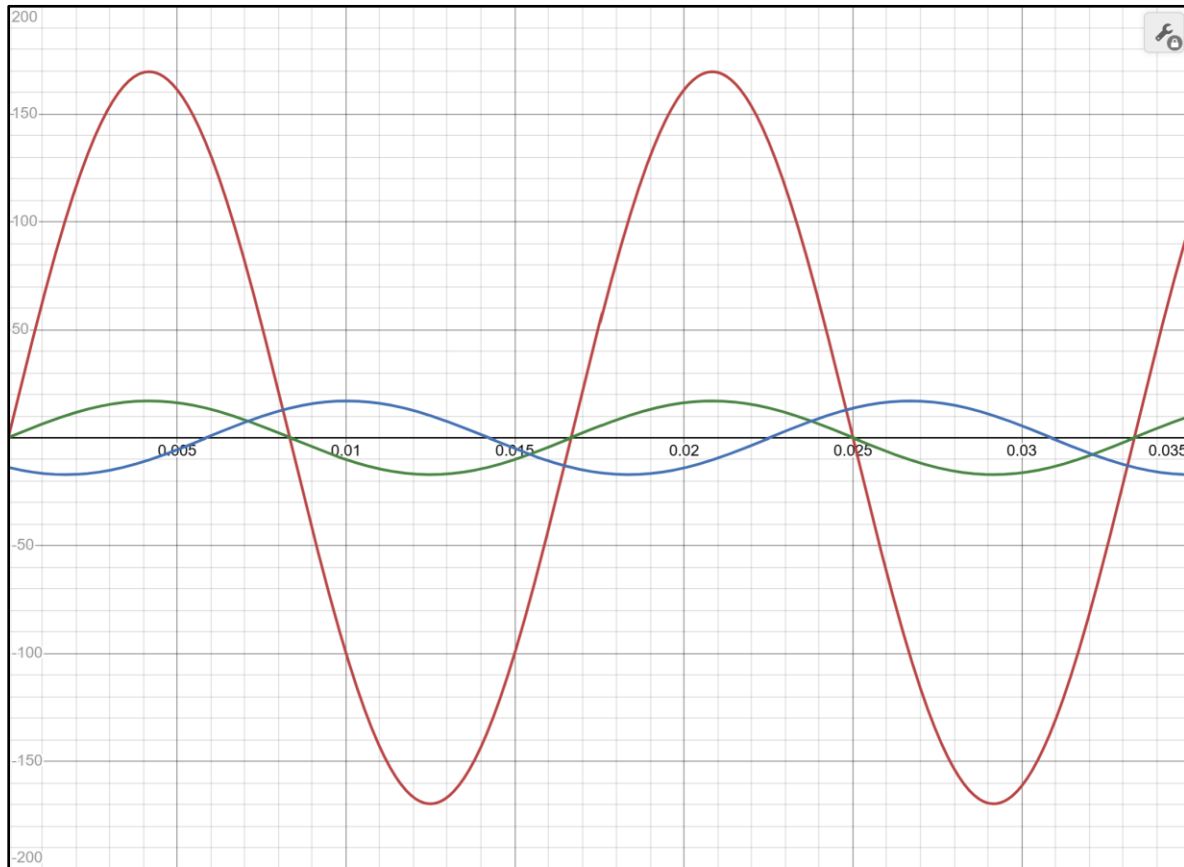


Figure #2: $V_A(t)$, $V_B(t)$, and $V_C(t)$ Spanning Two Cycles

Figure 3 shows the bridge rectifier circuit schematic used for this lab.

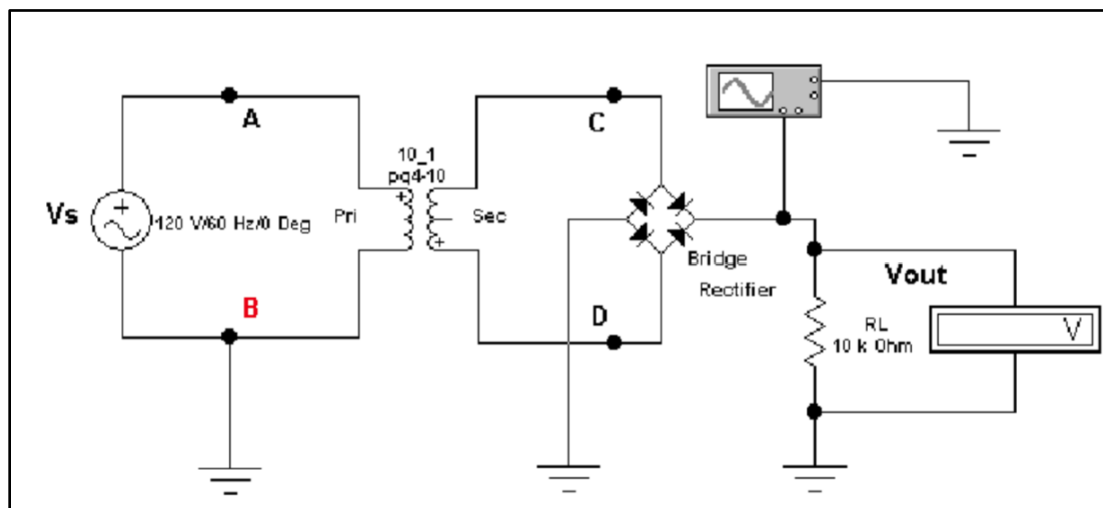


Figure #3: Bridge Rectifier Schematic (Lab Manual)

The ideal peak output voltage for the bridge rectifier circuit is approximately $V_{out,pk} = 16.97V$.

Using this peak output voltage, the DC value is roughly $V_{DC} = \frac{2V_{outpk}}{\pi} = 10.8V$. Using these values and the frequency, the following equation is formed:

$$V_{out}(t) = |16.97\sin(2\pi 60t)| V \quad (4)$$

A graph of Equation 4 spanning two cycles can be found in Figure 4. Node C contributes the odd number pulses while node D contributes the even number pulses.

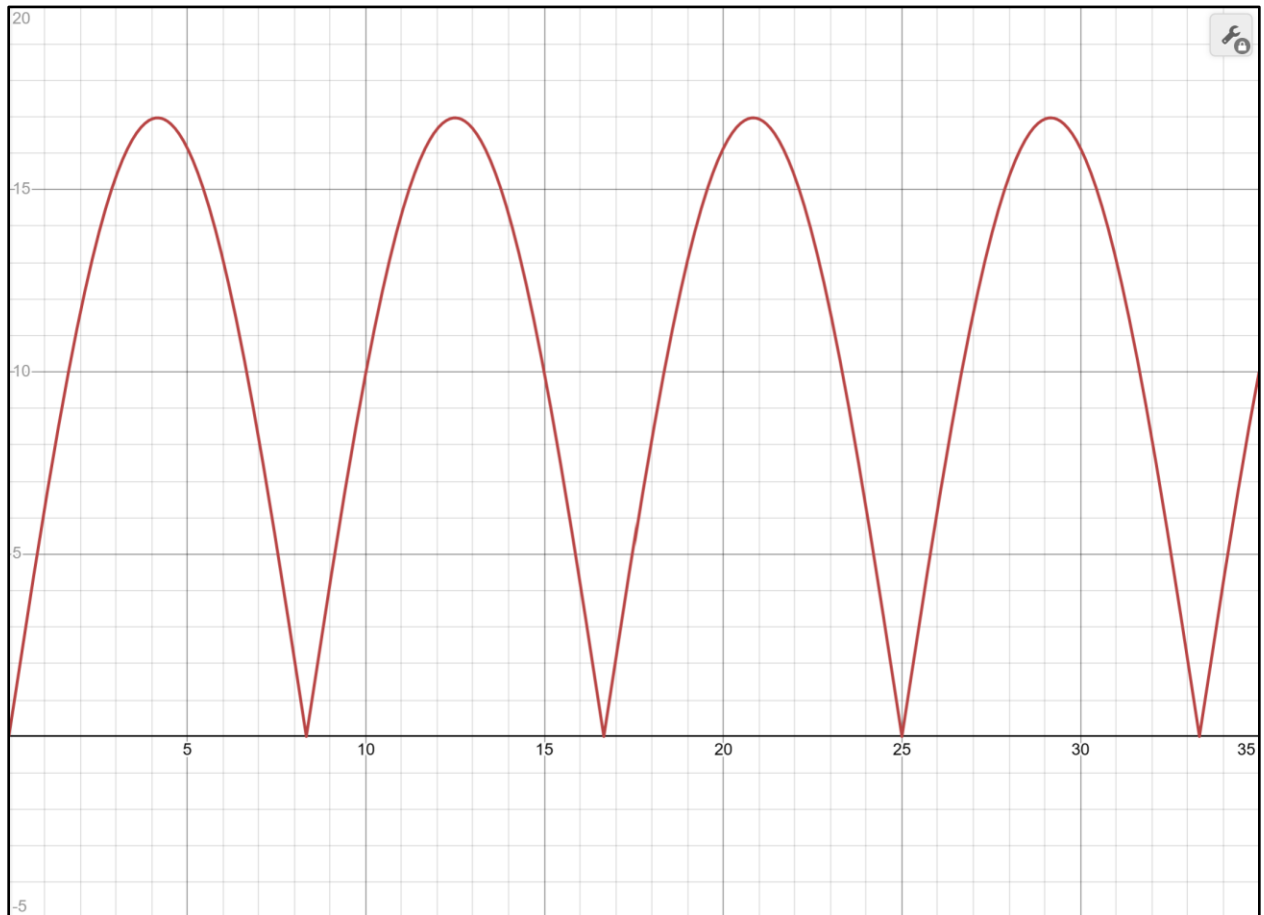


Figure #4: $V_{out}(t)$ Spanning Two Cycles

The ripple frequency f_{ripple} can be calculated using the input period $T_{in} = \frac{1}{60 \text{ Hz}} = 16.67 \text{ ms}$ and the output frequency $T_{out} = \frac{T_{in}}{2} = 8.33 \text{ ms}$.

$$f_{ripple} = \frac{1}{T_{out}} = 120 \text{ Hz}$$

If the circuit was a half rectifier instead of a full rectifier, the ripple frequency would be the same as the input frequency. In this case, the ripple frequency of the half rectifier would be 60 Hz.

Simulations and Results:

LTSpice was used to simulate two different transformer circuits, shown in Figures 1 and 3.

Figure 5 shows the basic transformer circuit in LTSpice. The Spice directive “K1 L1 L2 1” was used to show that the inductors L1 and L2 are perfectly coupled. A small input resistance was used to make the simulation non-ideal. Figure 6 shows the oscilloscope output of the primary and secondary voltages. The input sine wave has a peak voltage of 169.7V and the secondary output voltage has a peak of around 16.9V. The ratio between the inputs is roughly 0.01. Since the secondary voltage is expected to be around 10 times less than the input voltage, the simulation matches the expected results. The signals are also 180° out of phase with the maximum input voltage and minimum secondary voltages occurring at the same time. The frequency of the secondary coil was measured at 59.89 Hz, closely matching the input frequency of 60 Hz. Figure 7 shows the voltage differences between nodes A and D versus the differences between node C and ground. The results are the same as the first graph in Figure 6, with the two traces being 180° out of phase and the secondary voltage being 10 times less than the primary. In this second scenario, nodes A and C are producing the voltage while nodes B and D are acting as a common ground.

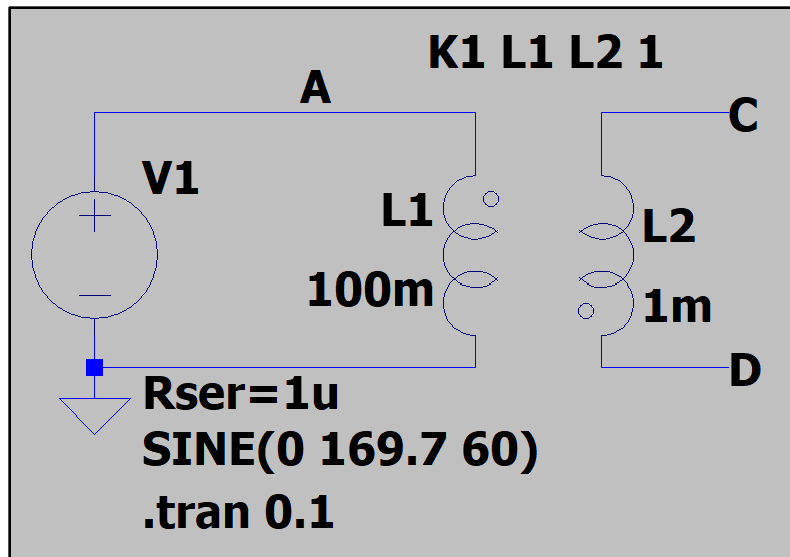


Figure #5: LTSpice Schematic (Basic Transformer)

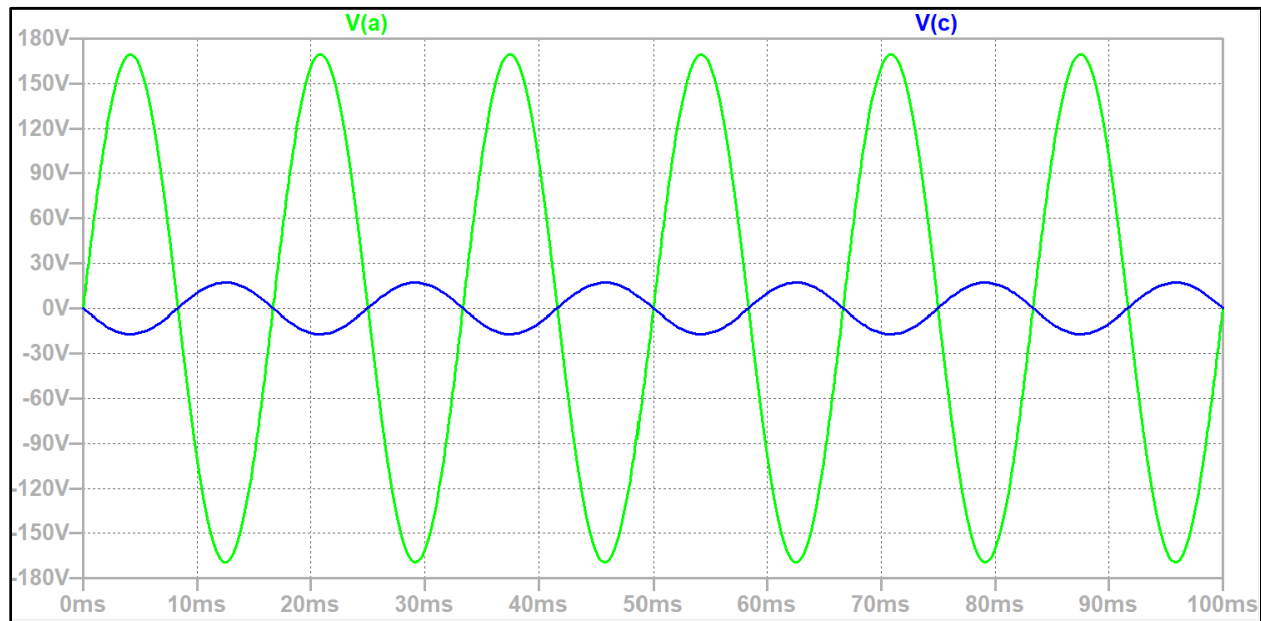


Figure #6: LTSpice Primary vs. Secondary Coil Voltage (Basic Transformer)

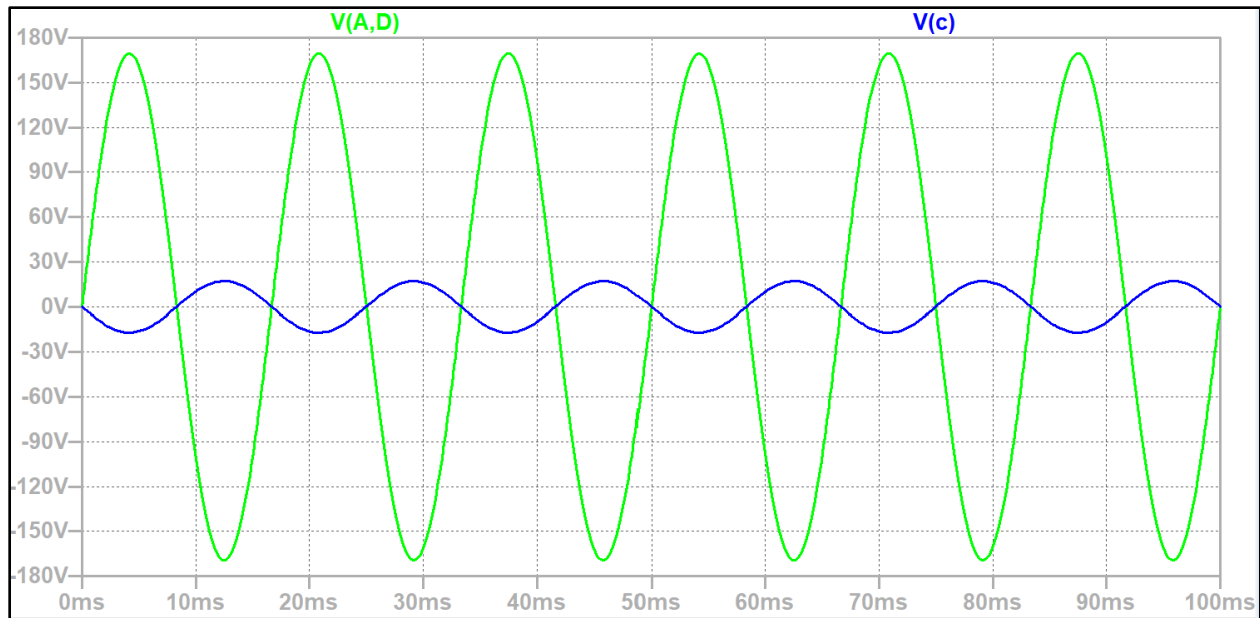


Figure #7: LTSpice Primary vs. Secondary Coil Voltage (Basic Transformer)

Figure 8 shows the bridge rectifier circuit in LTSpice. Figure 9 shows the oscilloscope output of the primary coil and rectified voltages. The rectified signal has a peak voltage of 15.629 V, or 11.051 V in DC. The period of the rectified voltage is about 8.325 ms, resulting in a frequency of 120 Hz.

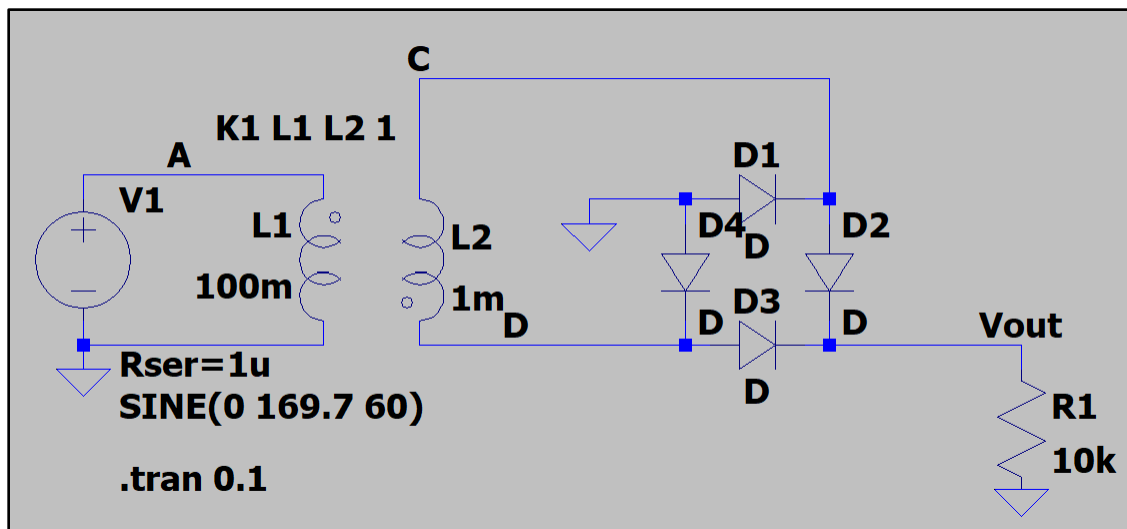


Figure #8: LTSpice Schematic (Bridge Rectifier)

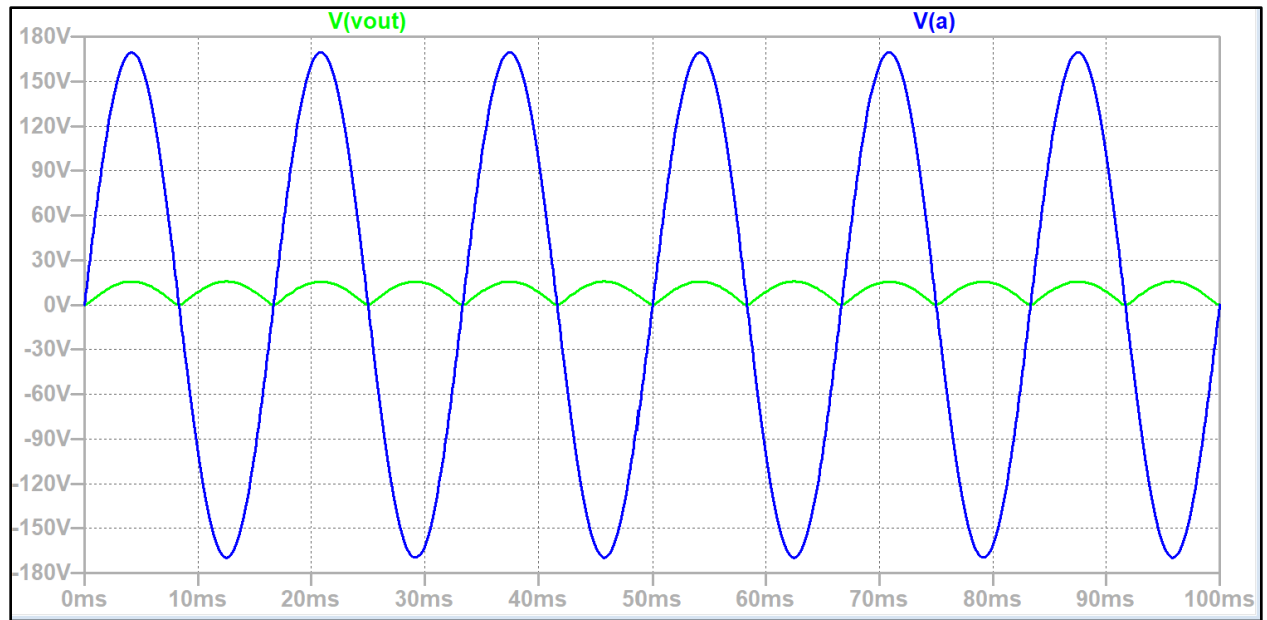


Figure #9: LTSpice Primary Coil vs. Rectified Voltages (Bridge Rectifier)